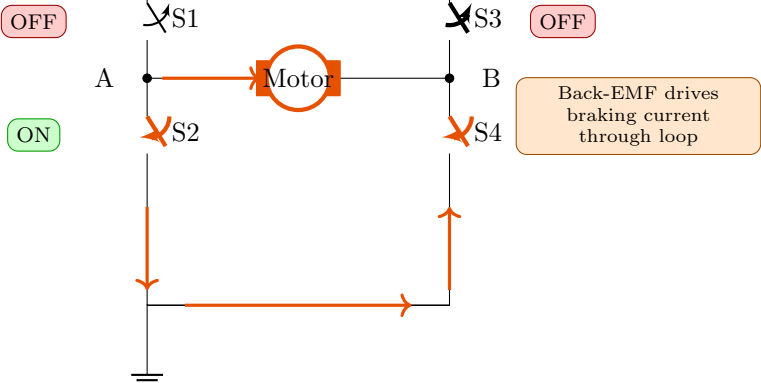


V_{motor}



OFF OFF

ON

Back-EMF drives braking current through loop

BRAKE: Motor terminals shorted